

# K-MAP for POS Expression

YADATI KRISHNA

August 30, 2022

## Contents

### 1 Components

### 2 Hardware

### 3 Software

#### Abstract

This manual shows how to use Arduino and LED to represent the K-MAP for POS expression for the function "G" shown in below truth table.

U	V	W	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

## 1 Components

Components	Value	Quantity
Arduino	UNO	1
LED	-	1
Jumper wires	M-M	3
Breadboard		1

## 2 Hardware

**Problem 2.1** Make connections between the Arduino and LED using Breadboard.

## 3 Software

**Problem 3.1.** execute the following program after downloading.

<https://github.com/KrishnaYadati/Assignments>

		VW			
		00	01	11	10
U	0	1	0	0	1
	1	1	0	1	0

#### K-MAP

U, V, W are the inputs and LED is the output. Using boolean logic.

$$G = (V + W')(U + W')(U' + V' + W) \quad (1)$$