

POS Expression for Paper 2013 Question 6)c

YADATI KRISHNA

August 23, 2022

Contents

1 Components

2 Hardware

3 Software

2 Hardware

Problem 2.1 Make connections between the Arduino and LED using Breadboard.

1

3 Software

1

Problem 3.1. Now make the connections as per Table 3.1 and execute the following program after downloading.

Abstract

This manual shows how to use Arduino with LED to represent POS expression.

<https://github.com/KrishnaYadati/Assignments>

1 Components

Components	Value	Quantity
Arduino	UNO	1
LED	-	1
Jumper wires	M-M	3
Breadboard		1

	W	V	U
Input	0	0	1
Arduino	8	7	6

U, V, W are the inputs and LED is the output. Using boolean logic,

$$G = (U+V+W')(U+V'+W')(U'+V+W')(U'+V'+W) \quad (1)$$